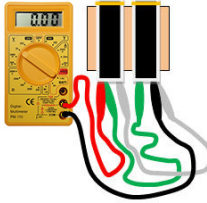
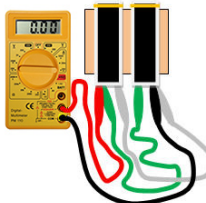
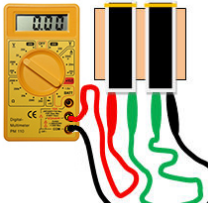
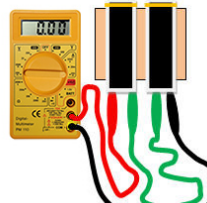
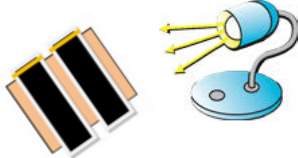
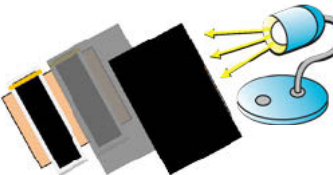
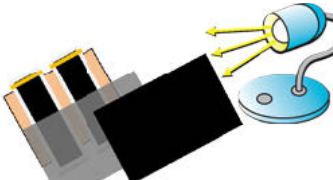


Worksheet 5: How do solar cells connected in series or in parallel behave when shaded?

Task 1

Conduct the experiment and enter the values you measure into the table.

	Parallel connection of the solar cells		Series connection of the solar cells	
	Voltage	Current	Voltage	Current
Shading of the solar cells				
Measurement	(V)	(mA)	(V)	(mA)
No shading 				
One solar cell is completely shaded 				
Both solar cells are half shaded 				

Task 2

Draw the circuit diagrams into the table. Use the circuit symbols.

Circuit diagrams

Circuit symbols		Parallel connection of solar cells		Series connection of solar cells	
		Voltage	Current	Voltage	Current
solar cell					
voltmeter					
ammeter					

Task 3

Describe the method of the experiment. Fill in the gaps of the text with the help of the words in the wordlist.

Wordlist

solar cell

light

black piece of paper

shading

voltage

current

measurement

table

2,000 mV

measured values

circuit diagram

measure

decrease

enter

draw

connect

hold

200 mA

shade

both

parallel

in series

completely

half

slightly

without

Conducting the experiment

First we connect the solar cells in parallel. Then we set the measuring range of the multimeter to

_____ and _____

Now we set the measuring range of the multimeter to _____

Then we connect the solar cells in series and repeat _____

Observation

With any kind of _____, the voltage only _____.

The current on the other hand _____ far more with shading. The _____

_____ is particularly strong when the solar cells are _____ in

_____ and one solar cells is shaded _____.