Worksheet 4 (answer sheet): Current and voltage with solar cells connected in series and in parallel

