

## 7.1 (1) Light dependent resistors (experiment with breadboard)




Find out about the properties of a light dependent resistor.



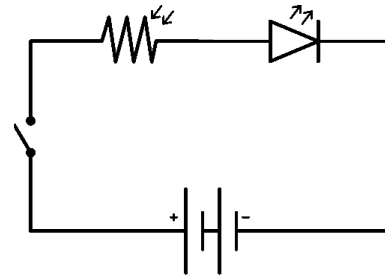
### Set up:

- Breadboard
- two 1.5 volt batteries
- cables
- LDR



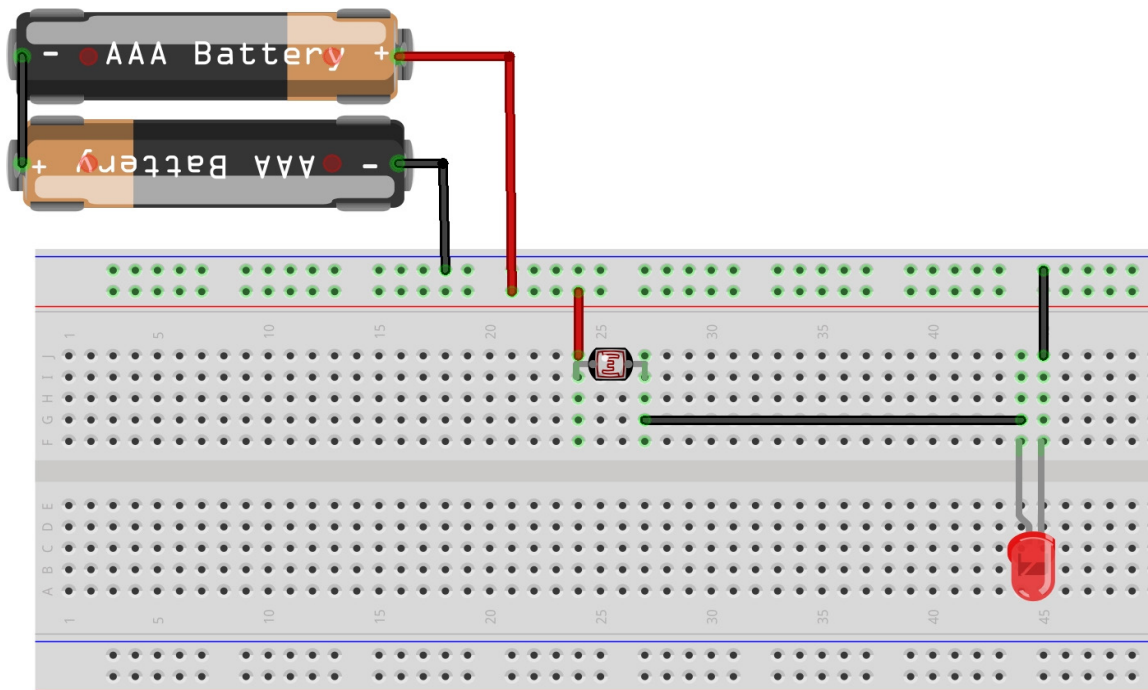1. Build the circuit as shown in the diagram.
2. Cover the LDR with your finger.



### Observing and documenting:

---



---



---



---



---



---



---



Analysing and reflecting:

---

---

---

---

---

---

---



How can you use the digital multimeter to test the properties of the LDR?

### Space for your sketches